

## Part I: Problems

Show working.

1. A  $315\ \mu\text{F}$  capacitor has dielectric (dielectric constant of 2.90) filling the  $0.275\ \text{mm}$  gap between its parallel plates. The charge on each plate has magnitude  $0.167\ \mu\text{C}$ . What is the magnitude of the surface charge density on each plate?

- a)  $17\ \text{pC/m}^2$
- b)  $49\ \text{pC/m}^2$
- c)  $94\ \text{pC/m}^2$
- d)  $140\ \text{pC/m}^2$


(2 points)

$$C = K\epsilon_0 \frac{A}{d} \implies A = \frac{C}{K\epsilon_0} d = 3.38 \times 10^3\ \text{m}^2 \implies \frac{|Q|}{A} = 4.9 \times 10^{-11}\ \text{C/m}^2$$

2. The three capacitors below are all fully charged. The charge on the  $1.0\ \mu\text{F}$  capacitor is  $2.0\ \mu\text{C}$ . What is the emf of the battery?

- a)  $1.7\ \text{V}$
- b)  $2.0\ \text{V}$
- c)  $2.3\ \text{V}$
- d)  $3.7\ \text{V}$

(4 points)

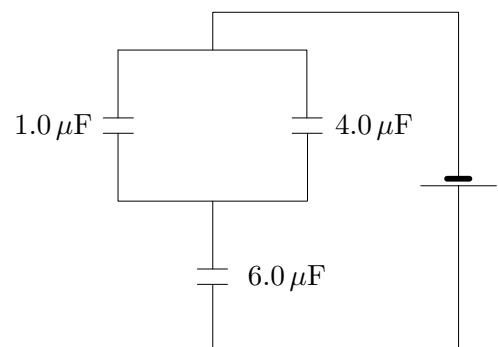

$$\begin{aligned} \Delta V_{1.0\ \mu\text{F}} = \frac{2.0\ \mu\text{C}}{1.0\ \mu\text{F}} = 2.0\ \text{V} = \Delta V_{4.0\ \mu\text{F}} &\implies Q_{4.0\ \mu\text{F}} = (4.0\ \mu\text{F})(2.0\ \text{V}) = 8.0\ \mu\text{C} \\ &\implies Q_{6.0\ \mu\text{F}} = Q_{1.0\ \mu\text{F}} + Q_{4.0\ \mu\text{F}} = 10.0\ \mu\text{C} \end{aligned}$$

$$\mathcal{E} = \Delta V_{4.0\ \mu\text{F}} + \Delta V_{6.0\ \mu\text{F}} = 2.0 + \frac{10.0\ \mu\text{C}}{6.0\ \mu\text{F}} = 3.7\ \text{V}$$

3. A wire (diameter of 1.95 mm) carries a current of 5.15 A; there are  $8.5 \times 10^{28}$  free electrons per cubic meter. How much time does a free electron take to travel a 1.25 m length of this wire?

- a)  $1.4 \times 10^3$  s  
 b)  $5.4 \times 10^3$  s  
 c)  $9.8 \times 10^3$  s  
 d)  $11 \times 10^3$  s


(2 points)

$$v_d = \frac{1}{nq} \frac{I}{A} = 1.27 \times 10^{-4} \text{ m/s} \implies \text{Time} = \frac{\text{Length}}{v_d} = 9.8 \times 10^3 \text{ s}$$

4. At  $20^\circ\text{C}$ , the cylindrical wire below carries a current of 2.65 A. What is the current at  $250^\circ\text{C}$  if the temperature coefficient of resistivity  $\alpha = 4.5 \times 10^{-3} (\text{C}^\circ)^{-1}$ ?

- a) 1.2 A  
 b) 1.3 A  
 c) 3.3 A  
 d) 3.4 A

(2 points)

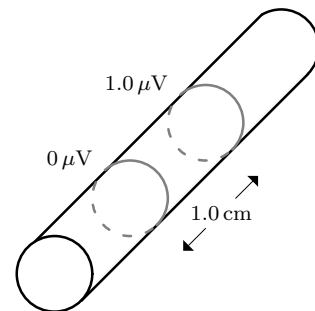


$$I_{250^\circ\text{C}} = \frac{\Delta V}{R_{250^\circ\text{C}}} = \frac{R_{20^\circ\text{C}}}{R_{250^\circ\text{C}}} I_{20^\circ\text{C}} \implies I_{250^\circ\text{C}} = \frac{\rho_{20^\circ\text{C}}}{\rho_{250^\circ\text{C}}} I_{20^\circ\text{C}} = \frac{1}{1 + (230^\circ\text{C})\alpha} I_{20^\circ\text{C}} = 1.3 \text{ A}$$

5. What is the potential difference  $V_a - V_b$  in the 2-loop circuit below?

- a)  $-6.3 \text{ V}$
- b)  $-9.8 \text{ V}$
- c)  $-14 \text{ V}$
- d)  $-23 \text{ V}$

(4 points)

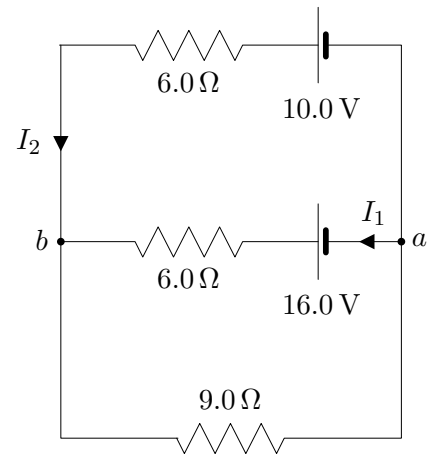

2 loop equations:

$$16 \text{ V} - 6I_1 + 6I_2 - 10 \text{ V} = 0 \quad \Rightarrow \quad I_2 = I_1 - 1$$


$$16 \text{ V} - 6I_1 - 9(I_1 + I_2) = 0 \quad \Rightarrow \quad 15I_1 + 9I_2 = 16 \text{ V}$$

$$\text{Solution for } I_1 : I_1 = \frac{25}{24} = 1.04 \text{ A} \quad \Rightarrow \quad V_a - V_b = +6I_1 - 16 \text{ V} = -9.8 \text{ A}$$

6. First, switch  $S_1$  below is closed for 5.0 ms and then opened; thereafter, switch  $S_2$  is closed. The capacitor was initially uncharged. What is the plate charge of the capacitor 5.0 ms after  $S_2$  is closed?

- a)  $21 \mu\text{C}$
- b)  $34 \mu\text{C}$
- c)  $73 \mu\text{C}$
- d)  $120 \mu\text{C}$

(3 points)

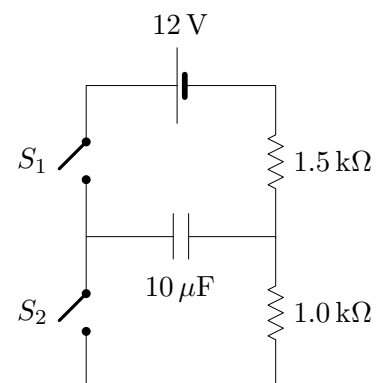


$$\text{Plate charge after charging: } Q_0 = (120 \mu\text{C}) \left[ 1 - \exp\left(-\frac{5 \text{ ms}}{15 \text{ ms}}\right) \right] = 34 \mu\text{C}$$

$$\text{Plate charge after discharging: } Q = 34 \mu\text{C} \exp\left(-\frac{5 \text{ ms}}{10 \text{ ms}}\right) = 20.6 \mu\text{C}$$

7. An electron moves along the  $x$ -axis shown away from a uniform ring of charge  $-7.5 \text{ pC}$  (radius  $a = 0.25 \text{ m}$ ) in the  $yz$ -plane. What is the speed of the electron at  $0.40 \text{ m}$  from the origin if the electron was released from rest at  $x = 0.20 \text{ m}$ ?

- a)  $43 \text{ km/s}$   
 b)  $120 \text{ km/s}$   
 c)  $150 \text{ km/s}$   
 d)  $220 \text{ km/s}$

(3 points)

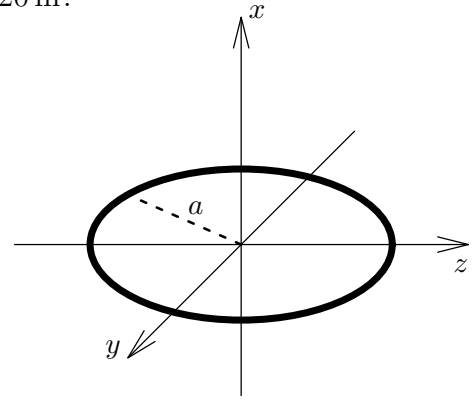

$$\Delta KE = -(-e)\Delta V = e \Delta \left( \frac{kQ}{\sqrt{a^2 + x^2}} \right) = 1.08 \times 10^{-20} \text{ J}$$

$$\Rightarrow v_{0.4 \text{ m}}^2 = \frac{2}{m_e} \Delta KE = 2.37 \times 10^{10} \text{ m/s} \Rightarrow v_{0.4 \text{ m}} = 154 \text{ km/s}$$

8. A charge ( $Q = +250 \text{ nC}$ ) is spread uniformly throughout the volume of a sphere (radius  $R = 35.0 \text{ cm}$ ). What is the potential at the center of the sphere if the potential is zero on the outer surface of the sphere?

- a)  $2.12 \text{ kV}$   
 b)  $3.21 \text{ kV}$   
 c)  $6.43 \text{ kV}$   
 d)  $9.64 \text{ kV}$

(2 points)


$$\begin{aligned} V_{\text{Outer surface}} - V_{\text{Center}} &= - \int_0^R E_r dr \Rightarrow V_{\text{Center}} = \int_0^R E_r dr = \int_0^R \frac{kQ}{R^3} r dr \\ &= \frac{kQ}{2R} = 3210 \text{ V} \end{aligned}$$

## Part II: Conceptual Questions

Tick (✓) the best answer.

1. For points  $A$ ,  $B$ ,  $C$  and  $D$  on the equipotentials below, the magnitude of the electric field is biggest at:





- ✓ a) A
- b) B
- c) C
- d) D

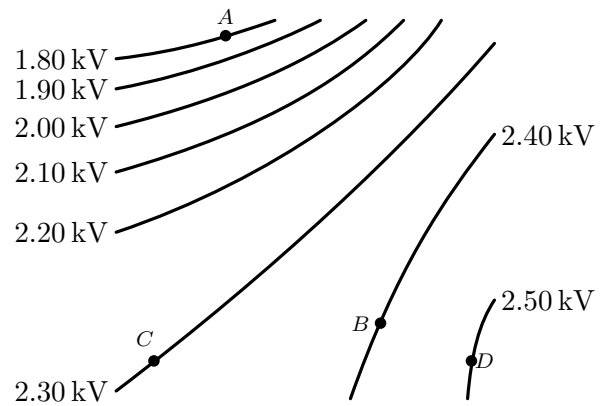

2. The electric potential (due to a charge distribution) is zero at some point  $P$ . Then,
- a) the electric field at  $P$  *must* be zero and the total charge in the region *must* be zero.
  - b) the electric field at  $P$  *must* be zero and the total charge in the region *may* be zero.
  - c) the electric field at  $P$  *may* be zero and the total charge in the region *must* be zero.
  - ✓ d) the electric field at  $P$  *may* be zero and the total charge in the region *may* be zero.

3. The potential differences  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_4$  across the four capacitors below are such that:

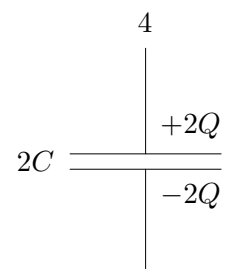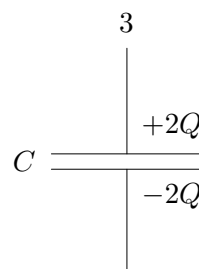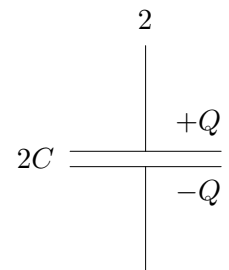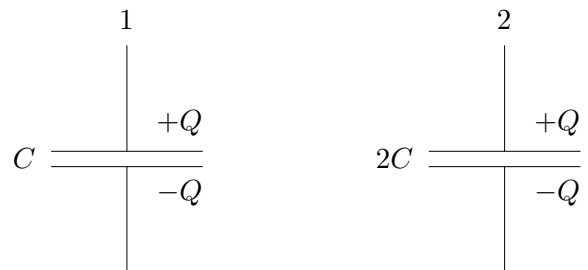
- a)  $V_3 = V_4 > V_1 = V_2$
- b)  $V_1 = V_3 > V_2 = V_4$
- ✓ c)  $V_3 > V_1 = V_4 > V_2$
- d)  $V_4 > V_2 = V_3 > V_1$



4. If a dielectric is inserted between the plates of an isolated charged capacitor (not connected to a battery), the energy stored in the capacitor
- a) always increases.
  - ✓ b) always decreases.
  - c) will increase for solids and decrease for fluids.
  - d) will decrease for solids and increase for fluids.


5. For points 1 and 2 in the current-carrying wire (of non-uniform cross-section) below, the correct statement is:

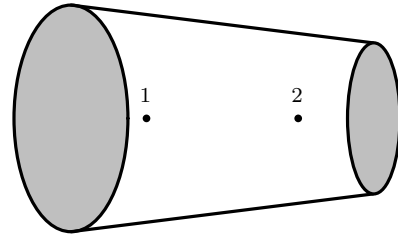- a)  $(v_d)_1 > (v_d)_2$
- b)  $\vec{E}_1 > \vec{E}_2$
- ✓ c)  $\vec{J}_1 < \vec{J}_2$
- d)  $I_1 < I_2$




6. In the circuit shown, the terminal voltage of the source 1 of emf is larger than  $\mathcal{E}_1$ . If  $r_1 = r_2$ , then:

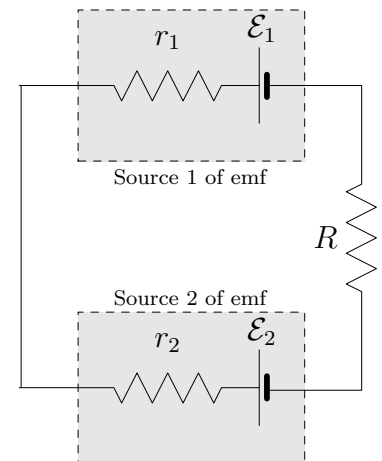- a)  $\mathcal{E}_1 > \mathcal{E}_2$  and the current is clockwise.
- b)  $\mathcal{E}_1 > \mathcal{E}_2$  and the current is anticlockwise.
- ✓ c)  $\mathcal{E}_1 < \mathcal{E}_2$  and the current is clockwise.
- d)  $\mathcal{E}_1 < \mathcal{E}_2$  and the current is anticlockwise.



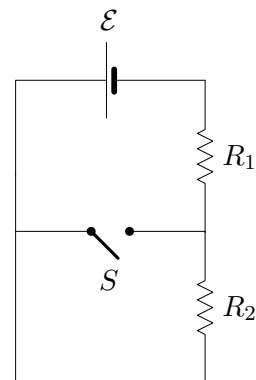7. If the switch  $S$  is closed in the circuit shown, the power dissipated in  $R_1$  will:

- ✓ a) increase.
- b) decrease.
- c) remain the same.
- d) become zero.



8. The graph shows the currents when 4 different capacitors (each with the same capacitance) are discharged separately through 4 different resistors. The largest resistance is:

- a)  $R_1$
- ✓ b)  $R_2$
- c)  $R_3$
- d)  $R_4$

