

**Problems - Show your solution in detail.**

1. Find the potential difference between points a and b shown in the figure.

Given  $C_1 = 1 \mu F$ ,  $C_2 = 2 \mu F$ ,  $C_3 = 3 \mu F$ ,  $C_4 = 4 \mu F$ ,  $C_5 = 5 \mu F$ , and  $V_2 = 12 V$ .


3 points

$$Q_1 = Q_2 = Q_3 = C_2 V_2 = 24 \mu C;$$

$$\Rightarrow V_1 = \frac{Q_1}{C_1} = \frac{24 \mu C}{1 \mu F} = 24 V$$


$$\Rightarrow V_3 = \frac{Q_3}{C_3} = \frac{24 \mu C}{3 \mu F} = 8 V$$

$$V = V_1 + V_2 + V_3 = 44 V$$

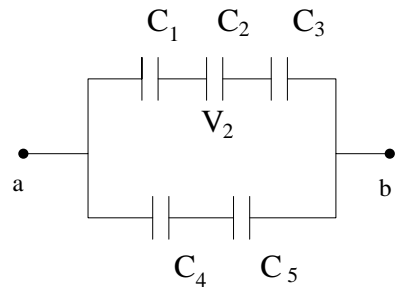

2. Capacitors  $C_1$  and  $C_2$  are connected in parallel with a battery. The magnitude of plate-charge in  $C_2$  ( $= 10 \mu F$ ) is  $Q_2 = 10 \mu C$ . The capacitance  $C_1$  and the charge  $Q_1$  are unknown. Then the battery is disconnected. After that a slab of dielectric material ( $K = 4$ ) is inserted between the plates of  $C_2$  and the charge in  $C_2'$  becomes  $Q_2' = 30 \mu C$ . Find the capacitance  $C_1$ .

4 points

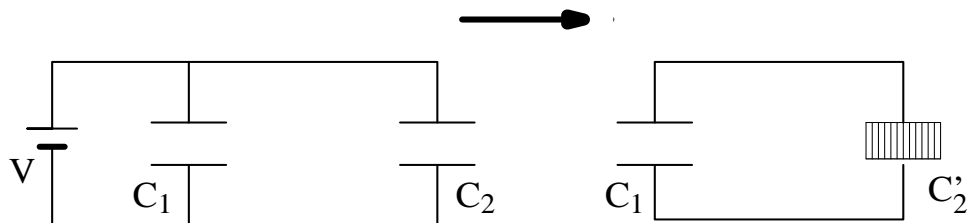

$$Q_2 = \frac{C_2 Q_{total}}{C_1 + C_2};$$


$$Q_2' = \frac{C_2' Q_{total}}{C_1 + C_2'}$$

$$3Q_2 = Q_2' \Rightarrow \frac{3C_2}{C_1 + C_2} = \frac{C_2'}{C_1 + C_2'} \Rightarrow \frac{3}{C_1 + C_2} = \frac{K}{C_1 + KC_2}$$

$$\text{so } 3(C_1 + 4C_2) = 4(C_1 + C_2) \Rightarrow C_1 = 80 \mu F$$

3. In the circuit shown, the switch S was closed for a very long time. Then at  $t = 0$  the switch is opened. Find the energy stored in the capacitor  $10\text{ ms}$  after the switch is opened. Given  $R_1 = R_2 = R_3 = 2\text{ k}\Omega$ , and  $C = 5\text{ }\mu\text{F}$ .

3 points

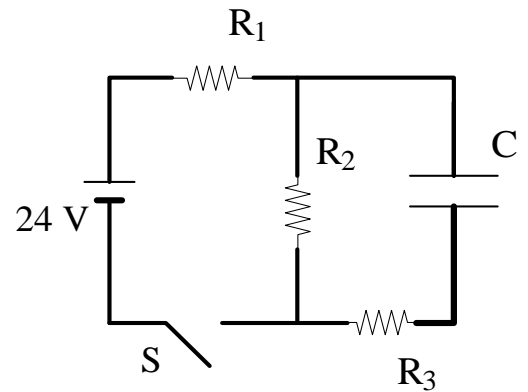


$$V_{C0} = 12\text{ V} \Rightarrow Q_0 = 5\mu\text{F} \cdot 12\text{V} = 60\mu\text{C}$$

$$\tau = 2RC = 20\text{ ms} \quad Q(10\text{ms}) = Q_0 e^{-\frac{10\text{ms}}{20\text{ms}}} = 36\mu\text{C}$$

$$U(10\text{ms}) = \frac{Q^2(10\text{ms})}{2C} = 132\mu\text{J}$$

4. In the circuit shown,  $R_1 = 1\text{ }\Omega$ ,  $R_2 = 2\text{ }\Omega$ ,  $R_3 = 3\text{ }\Omega$ ,  $\mathcal{E}_1 = 4\text{ V}$ , and  $\mathcal{E}_2 = 6\text{ V}$ . What is the rate of energy dissipation in the resistor  $R_1$ ?

5 points

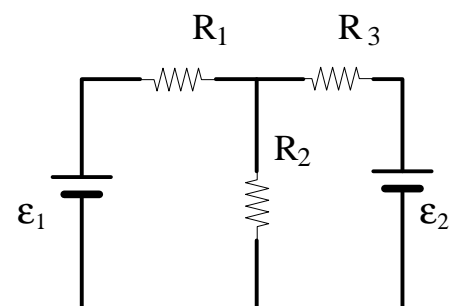

$$\text{junction rule: } i_1 + i_3 = i_2$$

$$\text{loop left: } 4\text{V} - i_1 R_1 - i_2 R_2 = 0$$

$$\text{loop right: } i_2 R_2 + i_3 R_3 - 6\text{V} = 0$$

For finding  $i_1 = 0.73\text{ A}$

$$p = i^2 R = 0.53\text{ W}$$

5. A copper wire of radius  $2 \text{ mm}$  carries a current of  $12 \text{ A}$ . The density of charge carriers is  $8.5 \times 10^{28} \text{ m}^{-3}$ . Find the drift speed of the electrons in the wire.

2 points

$$J = \frac{I}{A} = \frac{12 \text{ A}}{\pi r^2} = 9.5 \times 10^5 \text{ A/m}^2$$
$$v_d = \frac{J}{nq} = 7 \times 10^{-5} \text{ m/s}$$

6. At  $45^\circ \text{C}$  the resistance of a segment of a gold wire is  $85 \Omega$ . When the wire is placed in a liquid bath the resistance decreases to  $80 \Omega$ . What is the temperature of the liquid bath? Given  $\alpha = 3.4 \times 10^{-3} (\text{C}^\circ)^{-1}$ .

2 points

$$\frac{R}{R_0} = \frac{80}{85} = 1 + \alpha(T - T_0)$$
$$\Rightarrow T - T_0 = -17.3^\circ \text{C} \rightarrow T = 27.7^\circ \text{C}$$

7. A proton moves in a uniform magnetic field  $\vec{B} = (\vec{i} + 2\vec{j} - \vec{k}) T$ . At the instant when its velocity is  $\vec{v} = (2\vec{i} - 4\vec{j} + \vec{k}) m/s$ , what is the magnitude of the magnetic force on this proton?

3 points

By writing out the vector product :

$$\vec{v} \times \vec{B} = (2\hat{i} + 3\hat{j} + 8\hat{k}) \text{ mT/s}$$

$$|\vec{v} \times \vec{B}| = \sqrt{77} \text{ mT/s} = 8.8 \text{ mT/s}$$

$$F = q |\vec{v} \times \vec{B}| = 1.4 \times 10^{-18} \text{ N}$$


8. A wire consisting of two semicircular segments (with radii  $R_1 = 0.3 \text{ m}$  and  $R_2 = 0.9 \text{ m}$ ), as shown in the figure, carries a current of  $I = 3 \text{ A}$ . The wire is in a uniform magnetic field  $B = 2 \text{ T}$ , out of the page. Find the magnitude of the net magnetic force acting on the wire.

3 points

$$F_1 = I 2R_1 B = 3.6 \text{ N}$$

$$F_2 = I 2R_2 B = 10.8 \text{ N}$$

$$F = F_2 - F_1 = 7.2 \text{ N}$$

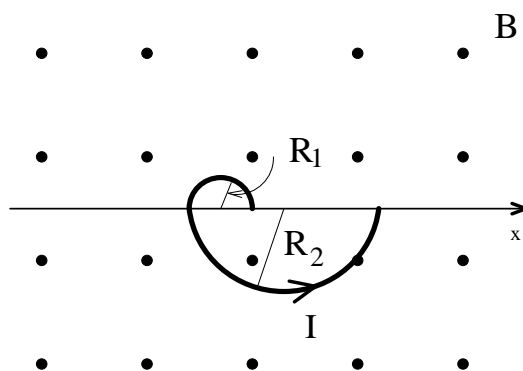


**Conceptual Question – Tick the correct answer (One point each)**

1. The electric field in a resistor connected to a battery is

- a. inversely proportional to the resistance of the resistor.
- b. proportional to the potential difference across the resistor.**
- c. inversely proportional to the current density.
- d. none of the above.


2. Three parallel-plate capacitors A, B, and C have the same geometrical parameters  $A$ ,  $d$  and have equal plate-charge  $Q$ . Different fractions of the space between the plates are filled with a dielectric material ( $K=3$ ) as shown in the figure. Rank the capacitors according to their potential differences. Smallest first.

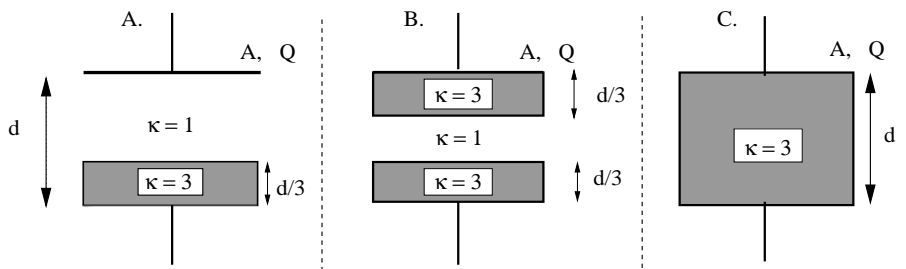- a. A, B, C
- b. C, B, A**
- c. B, C, A
- d. A, C, B




3. Rank the arrangement of resistors according to their equivalent resistances between the points a and b. Greatest first.

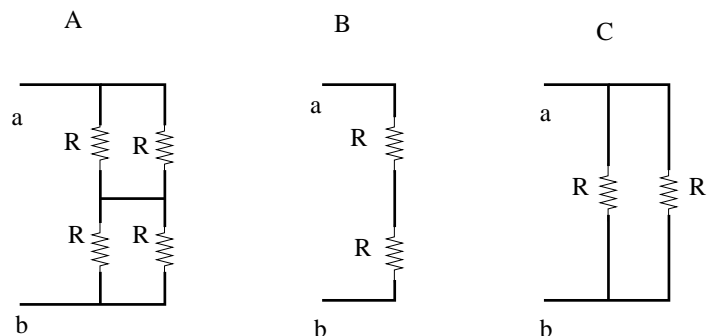- a. B, C, A.
- b. A, C, B.
- c. B, A, C.**
- d. A, B, C.




4. Three cylindrical copper wires with different lengths and cross-sectional areas are connected to the same potential differences. Rank the wires according to the power dissipated in them. Greatest first.

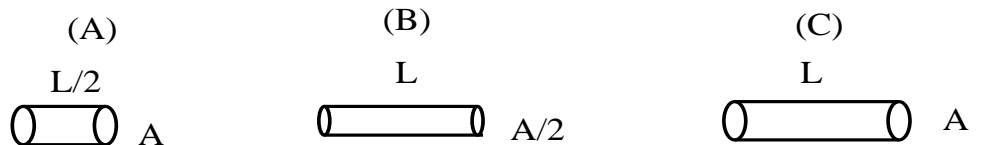- a. A, B, C,
- b. B, C, A,
- c. A, C, B,**
- d. C, B, A,



5. In the circuits shown, the resistances  $R$ , the capacitances  $C$  and the emfs  $\epsilon$  have the same values. Rank the circuits according to the charges stored in the capacitor. Greatest first.

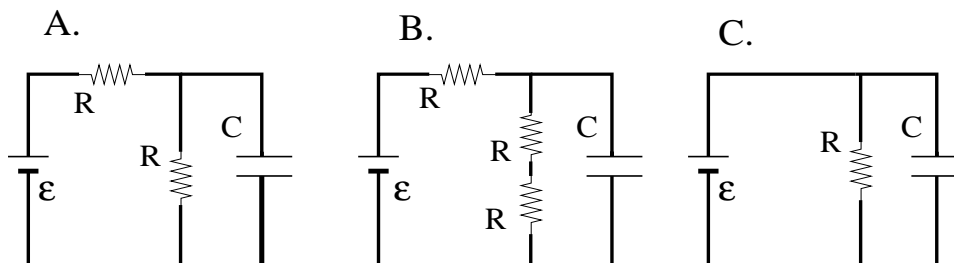- a. B. A. C.
- b. B. C. A.
- c. C. A. B.
- d. C. B. A.**




6. The temperature coefficient of resistivity of carbon is negative. Which statement is true for a resistor made of carbon at temperatures  $T_1$  and  $T_2$  ( $T_1 < T_2$ )?

- a.  $R(T_1) < R(T_2)$
- b.  $R(T_1) = R(T_2)$
- c.  $R(T_1) > R(T_2)$**
- d. There is not enough information to decide.

7. A positively charged particle projected into a very large a region of magnetic field  $\mathbf{B}$ , as shown in the figure will be. The particle will

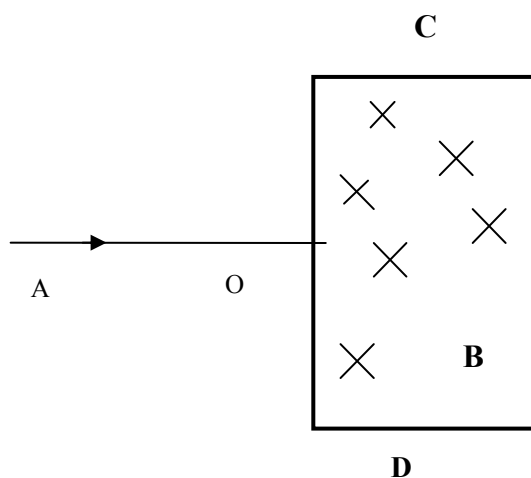- a) move straight without deflection.
- b) be deflected perpendicular to the direction AO and will reach the point C.
- c) be deflected perpendicular to the direction AO and will reach the point D.
- d) make a U turn.**



8. A wire having a mass  $M$  carries a current  $I$  in gravitational field, as shown in the figure. What is the direction of the magnetic field that can lift the wire up?

- a. Along the  $+y$  axis.
- b. Along the  $-y$ -axis.
- c. Along the  $+z$ -axis.**
- d. Along the  $-z$ -axis.

