



Kuwait University

Physics Department

Physics 102

Second Midterm Examination

Fall Semester (2011 - 2012)

December 14, 2011

Time: 12:30 – 1:45 PM

Name.....Student No.....

Instructors: Drs. Abdel-Karim, Afrousheh, Davis, Farhan, Kokaj, Lajko,

_____ Marafi, Pichler, Rakhshani, Razee and Sharma_____

(Fundamental constants)

$$k = \frac{1}{4\pi\epsilon_0} = 9.0 \times 10^9 \text{ Nm}^2 / \text{C}^2$$

(Coulomb constant)

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 / (\text{Nm}^2)$$

(Permittivity of free space)

$$\mu_0 = 4\pi \times 10^{-7} \text{ Tm/A}$$

(Permeability of free space)

$$|e| = 1.60 \times 10^{-19} \text{ C}$$

(Elementary unit of charge)

$$N_A = 6.02 \times 10^{23}$$

(Avogadro's number)

$$g = 9.8 \text{ m/s}^2$$

(Acceleration due to gravity)

$$m_e = 9.11 \times 10^{-31} \text{ kg}$$

(Electron mass)

$$m_p = 1.67 \times 10^{-27} \text{ kg}$$

(Proton mass)

Prefixes of units

$$m = 10^{-3}$$

$$\mu = 10^{-6}$$

$$n = 10^{-9}$$

$$p = 10^{-12}$$

$$k = 10^3$$

$$M = 10^6$$

$$G = 10^9$$

$$T = 10^{12}$$

For use by Instructors only

| Prob. | 1 | 2 | 3 | 4 | 5 | 6 | Total |
|-------|---|---|---|---|---|---|-------|
| Marks | | | | | | | |

| Ques. | 1 | 2 | 3 | 4 | 5 | 6 | Total |
|-------|---|---|---|---|---|---|-------|
| Marks | | | | | | | |

Problems***Please show all working.***


1. Three capacitors and a battery are connected in a circuit as shown in the figure. Find the charge on capacitor C_2 . **[4 points]**

$$C_{12} = C_1 + C_2 = 4\mu F;$$

$$C_{123} = \frac{C_{12}C_3}{C_{12} + C_3} = 2\mu F$$

$$Q_{123} = C_{123}\mathcal{E} = 24\mu C = Q_{12}$$

$$Q_2 = Q_{12} / 2 = 12\mu C$$

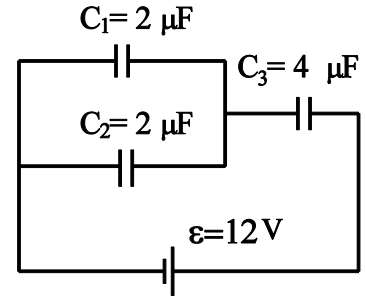

2. One third of the space between the plates of a parallel-plate capacitor is filled with a dielectric of dielectric constant $K=2$. The capacitance of this capacitor is $120\mu F$. Calculate the capacitance of the parallel-plate capacitor in the absence of the dielectric material. **[4 points]**


$$(C_0 \text{ is the capacitance without } K)$$

$$C_L = \frac{C_0}{3} K$$

$$C_R = \frac{2C_0}{3}$$

$$C_{eq} = C_L + C_R = C_0 \frac{4}{3} = 120\mu F \Rightarrow$$
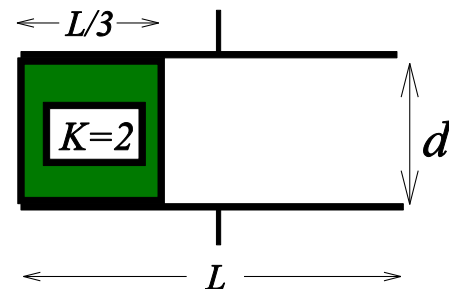
$$\Rightarrow C_0 = 120\mu F \frac{3}{4} = 90\mu F$$



3. A high voltage line of diameter 2 cm and length 20 km carries a steady current of 10 A. If the conductor has a free charge density of $8 \times 10^{28} \text{ m}^{-3}$, find how long it takes one electron to travel the full length of the cable. **[3 points]**

$$J = nev_d \Rightarrow v_d = \frac{J}{ne} = \frac{I}{Ane} = \frac{10A}{\pi(0.01m)^2 8 \times 10^{28} m^{-3} 1.6 \times 10^{-19} C} = 2.5 \times 10^{-6} m/s$$

$$t = \frac{L}{v_d} = \frac{2 \times 10^4 m}{2.5 \times 10^{-6} m/s} = 8 \times 10^9 s$$

4. In the circuit shown, find the power supplied to the circuit by the battery of emf ϵ_1 . **[5 points]**


$$\text{junction rule: } I_L + I_M = I_R$$

$$\text{left loop: } 4V - I_L 6\Omega + I_M 8\Omega = 0$$

$$\text{outer loop: } 14V + 4V - I_L 6\Omega - I_R 2\Omega = 0$$

$$\text{from which: } I_L = 2A$$


$$P = IV = 8W$$

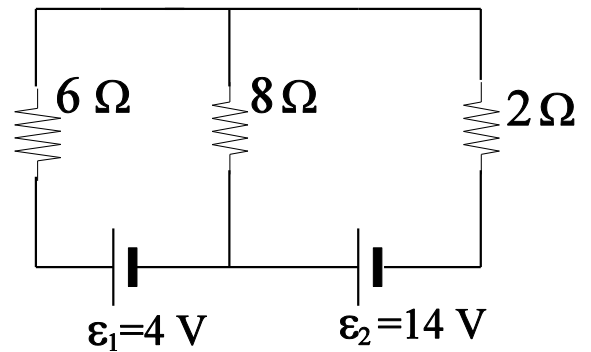

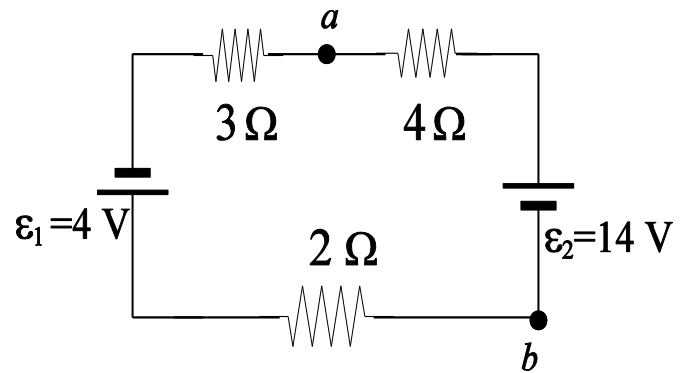
5. In the circuit shown, find the potential difference $V_a - V_b$.

[4 points]

$$\begin{aligned} 4V - I2\Omega + 14V - I4\Omega - I3\Omega &= 0 \\ I &= 2A \\ V_a + 2A \cdot 4\Omega - 14V &= V_b \\ V_a - V_b &= 6V \end{aligned}$$



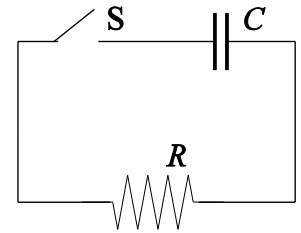6. In the circuit shown, the switch S is closed at $t=0$ and the capacitor C of initial charge Q_0 discharges via the resistor R .



(a) Derive an expression for the current in the circuit as a function of time.

$$I(t) = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-\frac{t}{RC}}$$

[2 points]

(b) Write an expression for the power dissipated in the resistor R as a function of time.

[1 point]

$$P = V(t)I(t) = \frac{Q_0}{C} e^{-\frac{t}{RC}} \frac{Q_0}{RC} e^{-\frac{t}{RC}} = \frac{Q_0^2}{RC^2} e^{-\frac{2t}{RC}}$$


(c) Write an integral for the energy dissipated in the resistor R between $t=0$ and $t = 10RC$ times.

[2 points]

$$E_{diss} = \int_0^{10RC} \frac{Q_0^2}{RC^2} e^{-\frac{2t}{RC}} dt$$

Conceptual questions. Each one point.**Tick (✓) the best answer.**

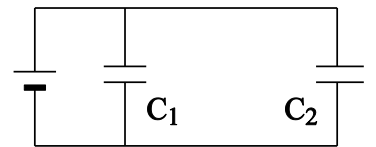1. A parallel-plate capacitor is charged and removed from the battery. When the plates are pulled apart, which of the following quantities decrease?
- (a) The electric field between the plates.
 - (b) The charge on the plates.
 - (c) The capacitance of the capacitor. **(Ans.)**
 - (d) The potential difference between the plates.
 - (e) The energy density of the electric field.
2. How does the resistance of a wire change if its length is doubled and its diameter is halved?
- a) Decreases by a factor of 2.
 - b) Increases by a factor of 2.
 - c) Increases by a factor of 4.
 - d) Increases by a factor of 8. **(Ans.)**
 - e) Remains the same.
3. Capacitors C_1 and C_2 ($C_1 < C_2$) are connected in parallel with a battery. Which of the following statement is true?
- (a) The potential difference across C_1 is greater than across C_2 .
 - (b) The potential differences across C_1 and C_2 are equal. **(Ans.)**
 - (c) The potential difference across C_2 is greater than across C_1
 - (d) The charges stored in C_1 and C_2 are equal.
 - (e) The charge stored in C_1 is larger than the charge stored in C_2 .



4. Which of the following is a correct Kichhoff junction rule equation for the currents in the circuit?


(a) $I_1 + I_2 + I_3 = 0$

(b) $I_1 + I_2 = I_3$

(c) $I_1 + I_3 = I_2$

(d) $I_2 + I_3 = I_1$ (Ans.)

(e) None of the above is correct.

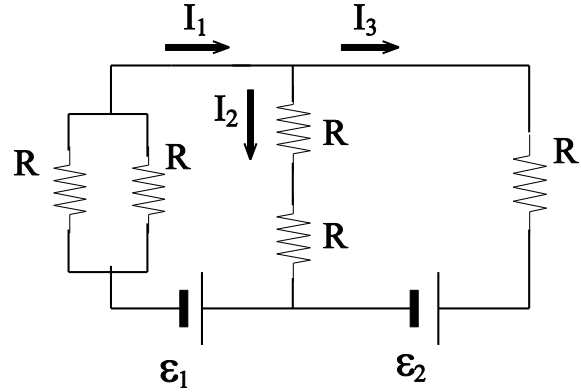

5. Long time after the switch S is closed, the current in the $15\text{-}\Omega$ resistor is


a) 2.6 A .

b) 2.5 A .

c) 2.0 A .

d) 1.6 A .

e) 0.0 A . (Ans.)

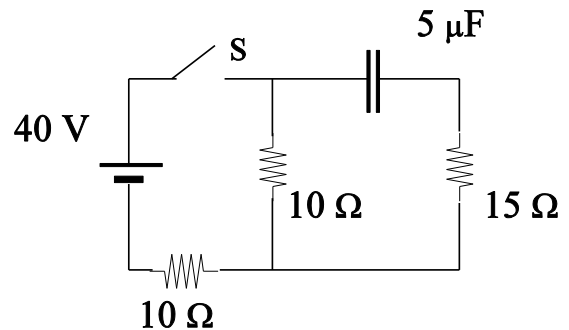

6. In the two separate R - C circuits the relation between the time constants τ_1 and τ_2 of circuits 1 and 2 is

(a) $\tau_1 = 0.25 \tau_2$.

(b) $\tau_1 = 0.5 \tau_2$. (Ans.)

(c) $\tau_1 = \tau_2$.

(d) $\tau_1 = 2 \tau_2$.

(e) $\tau_1 = 4 \tau_2$.

