



Physics 102

Second Midterm Examination

Spring Semester (2011-12)

May 5, 2012

Time: 12.00 to 1.30 p.m.

Name..... Student No.....

Instructors: Drs. Abdelkarim, Afrousheh, Davis, Farhan, Habib, Kokaj, Lajko,
Marafi, Razee & Sharma

(Fundamental constants)

$k = \frac{1}{4\pi\epsilon_0} = 9.0 \times 10^9 \text{ N}\cdot\text{m}^2 / \text{C}^2$	(Coulomb constant)
$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 / (\text{N}\cdot\text{m}^2)$	(Permittivity of free space)
$\mu_0 = 4\pi \times 10^{-7} \text{ T}\cdot\text{m/A}$	(Permeability of free space)
$ e = 1.60 \times 10^{-19} \text{ C}$	(Elementary unit of charge)
$N_A = 6.02 \times 10^{23}$	(Avogadro's number)
$g = 9.8 \text{ m/s}^2$	(Acceleration due to gravity)
$m_e = 9.11 \times 10^{-31} \text{ kg}$	(Electron mass)
$m_p = 1.67 \times 10^{-27} \text{ kg}$	(Proton mass)

Prefixes of units

$m = 10^{-3}$	$\mu = 10^{-6}$	$n = 10^{-9}$	$p = 10^{-12}$
$k = 10^3$	$M = 10^6$	$G = 10^9$	$T = 10^{12}$

For use by Instructors only

Prob.	1	2	3	4	5	6	7	8	Total
Marks									



Ques.	1	2	3	4	5	6	7	8	Total
Marks									

Problems

Please show ALL working.


1. Calculate the equivalent capacitance between points a and b .

[3 points]

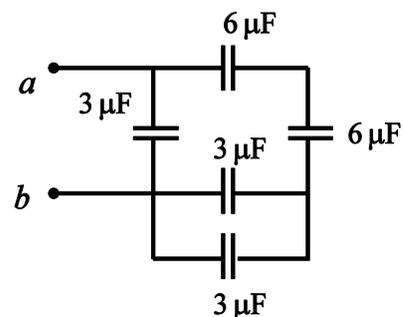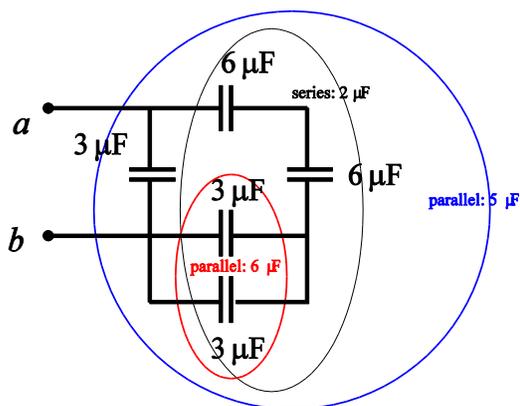

2. Identical capacitors ($C_1 = C_2 = 4 \mu\text{F}$) are connected together as shown. Each of the capacitors has an initial plate charge of $8 \mu\text{C}$. Then, a slab of dielectric material ($K = 3$) is inserted between the plates of C_2 fully filling the space between the plates. What is the final plate charge of C_1 ?

[3 points]

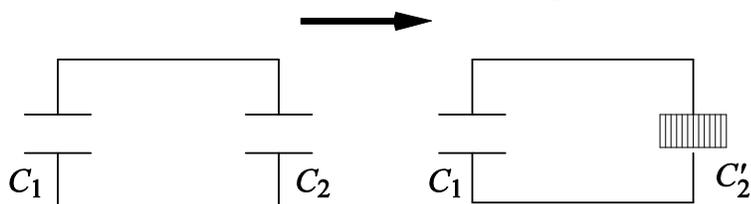

$$C'_{eq} = C_1 + C'_2 = 4 \mu\text{F} + 3 \cdot 4 \mu\text{F} = 16 \mu\text{F}$$

$$V' = \frac{8 \mu\text{C} + 8 \mu\text{C}}{C'_{eq}} = \frac{16 \mu\text{C}}{16 \mu\text{F}} = 1.0 \text{ V}$$

$$Q_1 = C_1 V' = 4 \mu\text{F} \cdot 1.0 \text{ V} = 4 \mu\text{C}$$

3. A parallel-plate capacitor has plate area $A = 0.5 \text{ m}^2$, plate separation $d = 0.1 \text{ mm}$ and energy density $u = 3.62 \text{ J/m}^3$. Find the plate charge on the capacitor. **[4 points]**

$$u = \frac{\epsilon_0}{2} E^2 = \frac{\epsilon_0}{2} \left(\frac{\sigma}{\epsilon_0} \right)^2 = \frac{1}{2\epsilon_0} \left(\frac{Q}{A} \right)^2$$

$$Q^2 = 2\epsilon_0 A^2 u$$

$$Q = \sqrt{2\epsilon_0 u} A = 4 \mu\text{C}$$

4. The electric field is $E = 0.1 \text{ V/m}$ in a cylindrical copper wire of resistivity $\rho = 1.72 \times 10^{-8} \Omega\text{m}$. The density of free electrons is $n = 8.5 \times 10^{28} / \text{m}^3$. Find the drift velocity of the electrons. **[3 points]**

$$\rho = \frac{E}{J} \Rightarrow nq v_d = J = \frac{0.1 \text{ N/C}}{1.72 \times 10^{-8}}$$


$$v_d = \frac{E}{\rho n q} = \frac{0.1 \text{ N/C}}{1.72 \times 10^{-8} \cdot 8.5 \times 10^{28} \cdot 1.6 \times 10^{-19}}$$
$$= 4.3 \times 10^{-4} \text{ m/s}$$

5. A cable consists of a solid cylinder (material 1, diameter = 10.0 mm) surrounded by a cylindrical shell (material 2, inner diameter = 10.0 mm, outer diameter = 20.0 mm). The cable carries a current of 100 A (parallel to its axis). If $\rho_1 = 2 \rho_2$, find the current density in the shell. [4 points]

$$I = J_1 A_1 + J_2 A_2 = \frac{\pi}{4} J_1 d_1^2 + \frac{\pi}{4} J_2 (d_2^2 - d_1^2)$$

$$\frac{J_2}{J_1} = \frac{E/\rho_2}{E/\rho_1} = \frac{\rho_1}{\rho_2} = 2$$
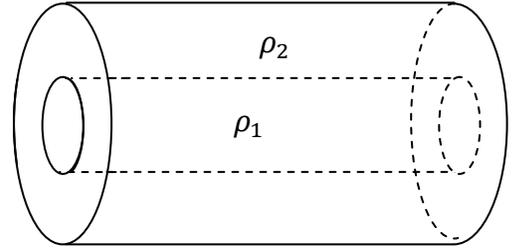
$$J_2 = I/\frac{\pi}{4} \left(d_2^2 - \frac{1}{2} d_1^2 \right) = 3.64 \times 10^5 \text{ A/m}^2$$




6. In the circuit below, the current through R_2 is 0.50 A. What is the terminal voltage of the source of emf with internal resistance r ? [4 points]

$$\text{Upper loop: } 0.5 \text{ A } R_2 - I_1 R_1 = 0$$

$$I_1 = 1.0 \text{ A}$$


$$I_1 + I_2 = I_3 = 1.5 \text{ A}$$
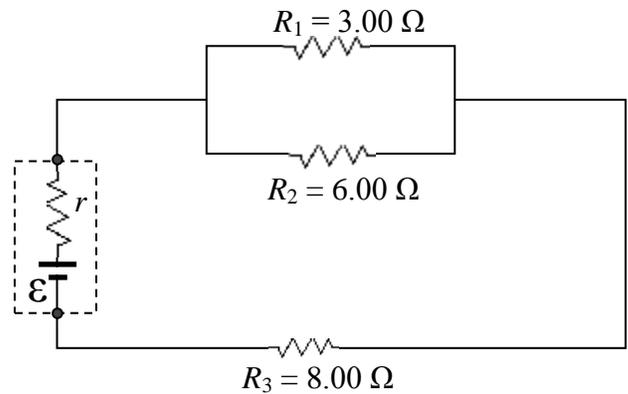
$$\text{Terminal voltage} = I_2 R_2 + I_3 R_3 = 15 \text{ V}$$



7. In the circuit shown, find the emf \mathcal{E}_1 and the resistance R .

[5 points]

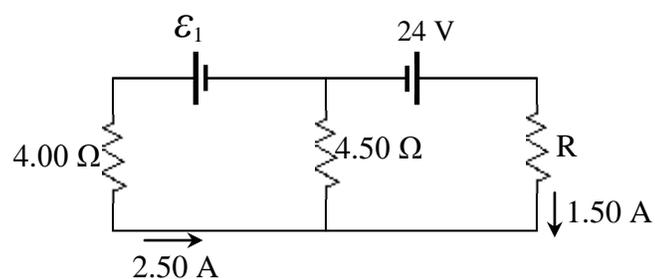

$$I_M = 2.5 \text{ A} + 1.5 \text{ A} = 4 \text{ A}$$

$$\mathcal{E}_1 - 2.50 \text{ A} (4.00 \Omega) - 4 \text{ A} (4.50 \Omega) = 0$$

$$-1.50 R - 4 \text{ A} (4.50 \Omega) + 24 \text{ V} = 0$$

$$\mathcal{E}_1 = 28 \text{ V}, \quad R = 4.0 \Omega$$

8. In the circuit shown, the capacitors are initially uncharged. The switch S is closed at $t=0$.


Find the time at which the current in the resistor is $5.4 \times 10^{-4} \text{ A}$.

[6 points]

$$C_{eq} = 4 \mu\text{F}$$

$$\tau = RC_{eq} = 3\text{k}\Omega \times 4\mu\text{F} = 12 \text{ ms}$$
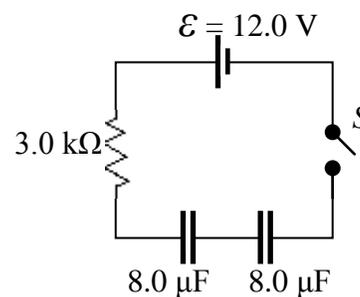
$$i = \frac{dq}{dt} = C\mathcal{E} \frac{d[1 - e^{-t/\tau}]}{dt} = \frac{\mathcal{E}}{R} e^{-t/\tau}$$



$$5.4 \times 10^{-4} \text{ A} = \frac{12\text{V}}{3\text{k}\Omega} e^{-t/\tau}$$

$$\Rightarrow \ln \left[\frac{5.4 \times 10^{-4}}{4 \times 10^{-3}} \right] = \frac{-t}{\tau} \Rightarrow t = -\tau \ln(0.135) = 24 \text{ ms}$$

Conceptual Questions. Tick the best answer. (1 point for each question.)

1. A parallel-plate capacitor is charged by a battery and kept connected to the battery. Then the separation between the plates is halved. How has the electric field in the capacitor changed?


- a. Decreased by a factor of 2.
- b. Increased by a factor of 2. **Ans.**
- c. Not changed.
- d. Increased by a factor of 4.

2. Two identical capacitors C_1 and C_2 have the same charge. Then we insert dielectric material ($K=3$) between the plates of C_2 . The ratio U_1/U_2 of the energies stored in C_1 and C_2 is

- a. 3. **Ans.**
- b. 1/3.
- c. 1.
- d. 9.

3. The figure shows a steady electric current I passing through a wire of changing cross-section. How does the drift velocity change?

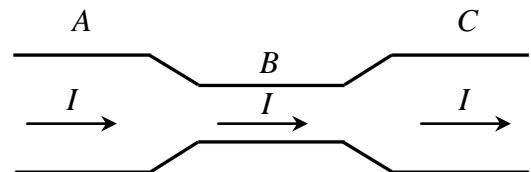- a. Decreases from A to B , increases from B to C .
- b. Decreases from left to right.
- c. Remains constant.
- d. Increases from A to B , decreases from B to C . **Ans.**



4. A potential difference V is applied to the two ends of a cylindrical wire. If the diameter of the wire is doubled and the potential difference V is halved, then the *rate* of energy dissipation in the wire


- a. remains the same. **Ans.**
- b. decreases by a factor of 2.
- c. increases by a factor of 4.
- d. increases by a factor of 2.
- e. decreases by a factor of 4.

5. Which combination below is a unit of energy?

- a) $A^2 \cdot \Omega$.
- b) $\Omega \cdot m$.
- c) $\frac{A}{C}$.
- d) $V \cdot C$. **Ans.**


6. A capacitor and resistor are connected to an emf as shown. Just after the switch S is closed, which of the following statements is true?

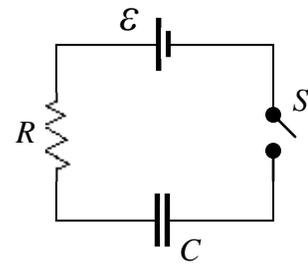- a) The current is zero.
- b) The voltage across the capacitor is ϵ .
- c) The voltage across the resistor is zero.
- d) The voltage across the resistor is ϵ . **Ans.**



7. A light bulb is connected in a circuit as shown. If the switch S is closed, the bulb's brightness

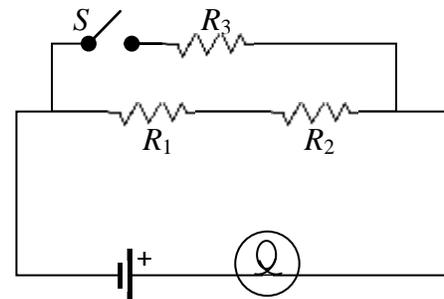- a) increases if $R_3 > R_1 + R_2$.
- b) decreases if $R_3 > R_1 + R_2$.
- c) always decreases.
- d) always increases. **Ans.**



8. The electrical properties of copper and rubber are different because:

- a) positive charges can move in copper but not in rubber.
- b) positive charges can move in rubber but not in copper.
- c) negative charges can move in copper but not in rubber. **Ans.**
- d) negative charges can move in rubber but not in copper.