



Physics 102

Second Midterm Examination

Summer Semester 2010-2011

July 16th, 2012

Time: 6:00 pm – 7:30 pm

Name..... Student No.....

Instructors: Drs. Abdelkarim, Afrousheh, Farhan, Kokaj,
Marafi, Rakhshani, Razee and Sharma.

(Fundamental constants)

$k = \frac{1}{4\pi\epsilon_0} = 9.0 \times 10^9 \text{ N}\cdot\text{m}^2 / \text{C}^2$	(Coulomb constant)
$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 / (\text{N}\cdot\text{m}^2)$	(Permittivity of free space)
$\mu_0 = 4\pi \times 10^{-7} \text{ T}\cdot\text{m/A}$	(Permeability of free space)
$ e = 1.60 \times 10^{-19} \text{ C}$	(Elementary unit of charge)
$N_A = 6.02 \times 10^{22}$	(Avogadro's number)
$g = 9.8 \text{ m/s}^2$	(Acceleration due to gravity)
$m_e = 9.11 \times 10^{-31} \text{ kg}$	(Electron mass)
$m_p = 1.67 \times 10^{-27} \text{ kg}$	(Proton mass)

Prefixes of units

$m = 10^{-3}$	$\mu = 10^{-6}$	$n = 10^{-9}$	$p = 10^{-12}$
$k = 10^3$	$M = 10^6$	$G = 10^9$	$T = 10^{12}$

For use by Instructors only

Prob.	1	2	3	4	5	6	7	8	Total
Marks									

Ques.	1	2	3	4	5	6	7	8	Total
Marks									

PART I: Solve the following Problems. Show your solution in detail.

1. Given that $C_1 = 50 \mu\text{F}$, $C_2 = 30 \mu\text{F}$, $C_3 = 36 \mu\text{F}$, $C_4 = 12 \mu\text{F}$, and $\mathcal{E} = 30 \text{ V}$. What is the energy stored in C_3 .


$$C_{234} = C_2 + C_3 + C_4 = 78 \mu\text{F}$$

$$C_{eq} = \frac{C_{234} \times C_1}{C_{234} + C_1} = 30.5 \mu\text{F}$$

$$Q = C_e \mathcal{E} = 915 \mu\text{C}$$

$$V_3 = V_{234} = \frac{Q}{C_{234}} = 11.7 \text{ V}$$
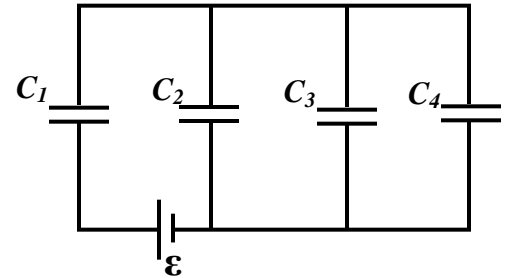
$$U_3 = \frac{1}{2} C V^2 = 2.47 \text{ mJ}$$



2. A $30 \mu\text{F}$ capacitor is charged to an unknown potential V and then connected in parallel with an initially uncharged $10 \mu\text{F}$ capacitor. If the final potential difference across the $10 \mu\text{F}$ capacitor is 20 V , determine the potential V .

$$C_{eq} = C_1 + C_2 = 40 \mu\text{F}$$

$$V_f = \frac{Q}{C_{eq}} = \frac{V C_1}{C_{eq}}$$

$$20 = V \frac{30}{40}$$

$$V = 27 \text{ V}$$

3. An isolated $240 \mu\text{F}$ air-filled parallel-plate capacitor is charged to $160 \mu\text{C}$. If a dielectric material ($K = 3.2$) is inserted filling one third of the space between the plates, as shown. Calculate the work done by the external agent in the process.


$$C_f = C_{air} + C_\kappa$$

$$C_{air} = \epsilon_o \frac{2A}{3d} = \frac{2}{3} C_i$$

$$C_\kappa = \kappa \epsilon_o \frac{A}{3d} = \frac{\kappa}{3} C_i$$

$$\Delta U = W_{ex} = \frac{Q^2}{2} \left(\frac{1}{C_f} - \frac{1}{C_i} \right)$$

$$\Delta U = -22.5 \mu\text{J}$$

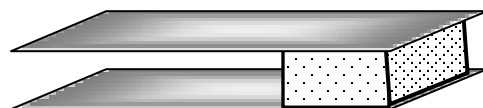

4. In a steady state current, how many electrons pass through a 20Ω resistor in 10 minutes if there is a potential difference of 30 volts across it?

$$Q = Ne$$

$$V/R = Q/t$$

$$N = 5.6 \times 10^{21}$$

5. Two real batteries with emf $\mathcal{E}_1 = \mathcal{E}_2 = \mathcal{E}$, but different internal resistances $r_1 = 0.5 \Omega$ and $r_2 = 0.3 \Omega$ are connected in series to an external resistance R . Find the value of R so the terminal voltage of \mathcal{E}_1 is zero.

$$0 = \mathcal{E} - ir_1$$

$$i = \frac{\mathcal{E}}{r_2 + R}$$

$$R = r_1 - r_2 = 0.2 \Omega$$

6. In the circuit shown the current in the 2Ω resistor is 2 A, as shown. Find the value of the emf \mathcal{E} .


$$-2 \times 2 + 12 - 1 \times I_3 = 0$$

$$I_3 = 8 \text{ A}$$

$$I_1 = I_3 - I = 6 \text{ A}$$

$$\mathcal{E} - 5I_1 - 1 \times I_3 = 0$$

$$\mathcal{E} = 38 \text{ V}$$

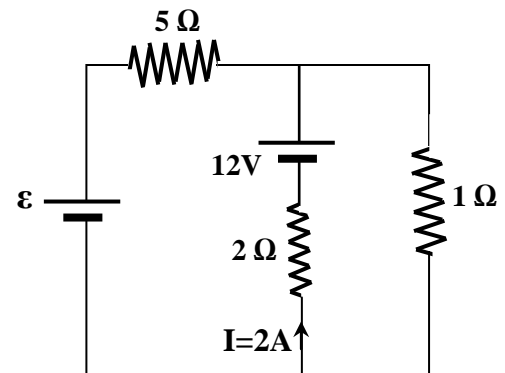

7. A conducting wire of 1.20 mm diameter carries a current of 3.00 A produced by an electric field of 120 V/m. Calculate the resistivity of the material.

$$R = \rho \frac{L}{A} = \frac{V}{I}$$

$$\rho = \left(\frac{A}{I} \right) \left(\frac{V}{L} \right) = \left(\frac{\pi r^2}{I} \right) E$$


$$\rho = \frac{\pi (0.6 \times 10^{-3})^2}{3} \times 120 = 4.52 \times 10^{-5} \Omega \cdot m$$

8. A charge of uniform density is distributed along the x axis from the origin to the point $x=10$ cm. If the electric potential (relative to zero at infinity) is 5.8V at $x = 18$ cm, what is the linear charge density?

$$V = \int_0^{10} k \frac{\lambda dx}{18-x}$$

$$V = -k\lambda \ln \frac{8}{18} = k\lambda(0.81)$$


$$\lambda = 0.8 \text{ nC/m}$$

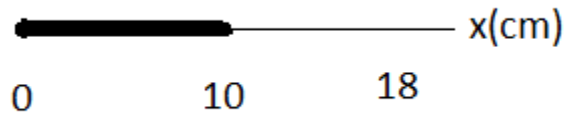

PART II: Conceptual Questions (1 point each). Tick the most suitable answer.

1. Relative to infinity, the potential at the center of a spherical charged conducting shell of radii a and b ($a < b$) carrying a charge Q is;

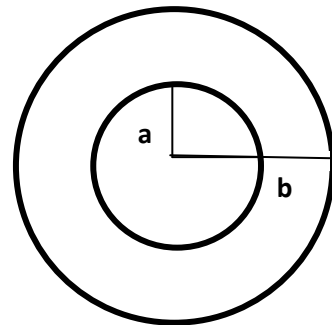- a) KQ/a
- b) KQ/b
- c) 0
- d) $KQ(1/a-1/b)$




2. The electrostatic energy density inside a capacitor is uniform. The capacitor must be

- a) a spherical capacitor.
- b) a cylindrical capacitor
- c) a parallel-plate capacitor.
- d) a capacitor of any shape.


3. When the switch S is closed, the current through R_3

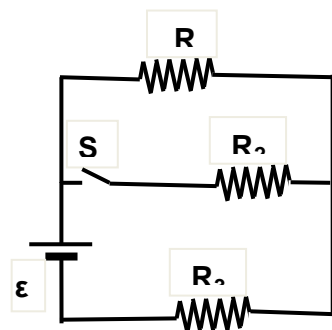- a) remains the same.
- b) increases.
- c) decreases.
- d) can only be determined by knowing the values of the resistances.




4. A conducting block of dimensions a , $b = a$ and $c = 3a$ is connected to an emf source \mathcal{E} in two different ways, as shown. Comparing the value of the drift velocity in the two cases (v_1 and v_2),

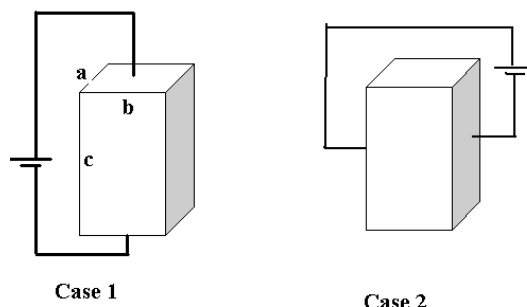- a) $v_1 = v_2$.
- b) $v_1 = 3 v_2$.
- c) $v_1 = v_2/3$
- d) $v_1 = 9v_2$.



5. You have three equal capacitors of capacitance 60 nF each. Which combination below yields an equivalent capacitance of 90 nF.

- a) A
- b) B
- c) C
- d) D

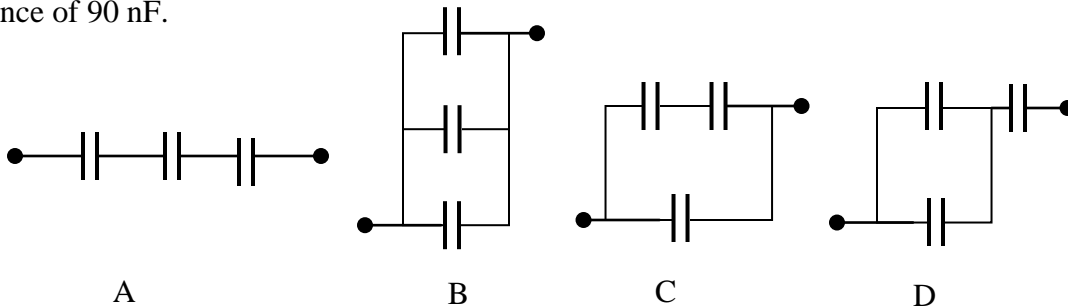

6. The junction Kirchhoff rule is a statement of

- a) energy conservation law.
- b) charge conservation law.
- c) Gauss' Law.
- d) Coulomb's Law.

7. An air-filled parallel plate capacitor made of two circular plates of radii a and separation d has a capacitance C . If the separation and the radii are decreased to half their initial values and a dielectric material of $K=2$ is inserted filling the whole region between the plates; the new capacitance is

- a) C .
- b) $2C$.
- c) $4C$.
- d) $C/2$.

8. For the circuit shown, all bulbs have the same resistance. Which bulb is brightest?

- a) A
- b) B
- c) C
- d) B and C

